

Electronics Lab 1

Andrew Rippy*

Department of Physics, Wabash College, Crawfordsville, IN 47933

(Dated: February 2nd, 2021)

The purpose of this lab was to create simple circuits, and see the voltage vs. current over 4 components; an LED, Germanium Diode, Lamp, and a resistor.

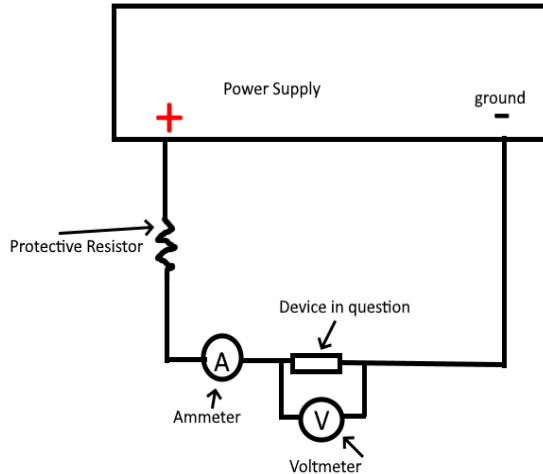


FIG. 1. The general circuit

I. INTRODUCTION

Using an ammeter and voltmeter, we measured the voltage and amps of the circuit component in question.

II. THEORETICAL MODEL

If the component is ohmic, it should follow Ohm's law,

$$V = IR \quad (1)$$

Thus, if the curve of the voltage vs. current is linear, it is ohmic, otherwise, it is not.

III. EXPERIMENT

A. Procedure

For the experiment we set up various simple circuits with a resistor in series with the component in question. The circuit was powered by a variable power supply, and the general form of the circuit is shown in Fig. 1.

B. Data

For each component, we ran current both forward and backward through the device. Units are in volts and mAmps, unless otherwise specified. See attached data.


IV. CONCLUSION

In conclusion: Resistors were found to be ohmic, LED's were found to not be ohmic, Diodes were found to not be ohmic, and Lamps were found to not be ohmic.

ACKNOWLEDGEMENTS


I acknowledge the support of the Wabash College Physics Department and Professor Brown's benevolence in these crazy times.

* anrippy22@wabash.edu

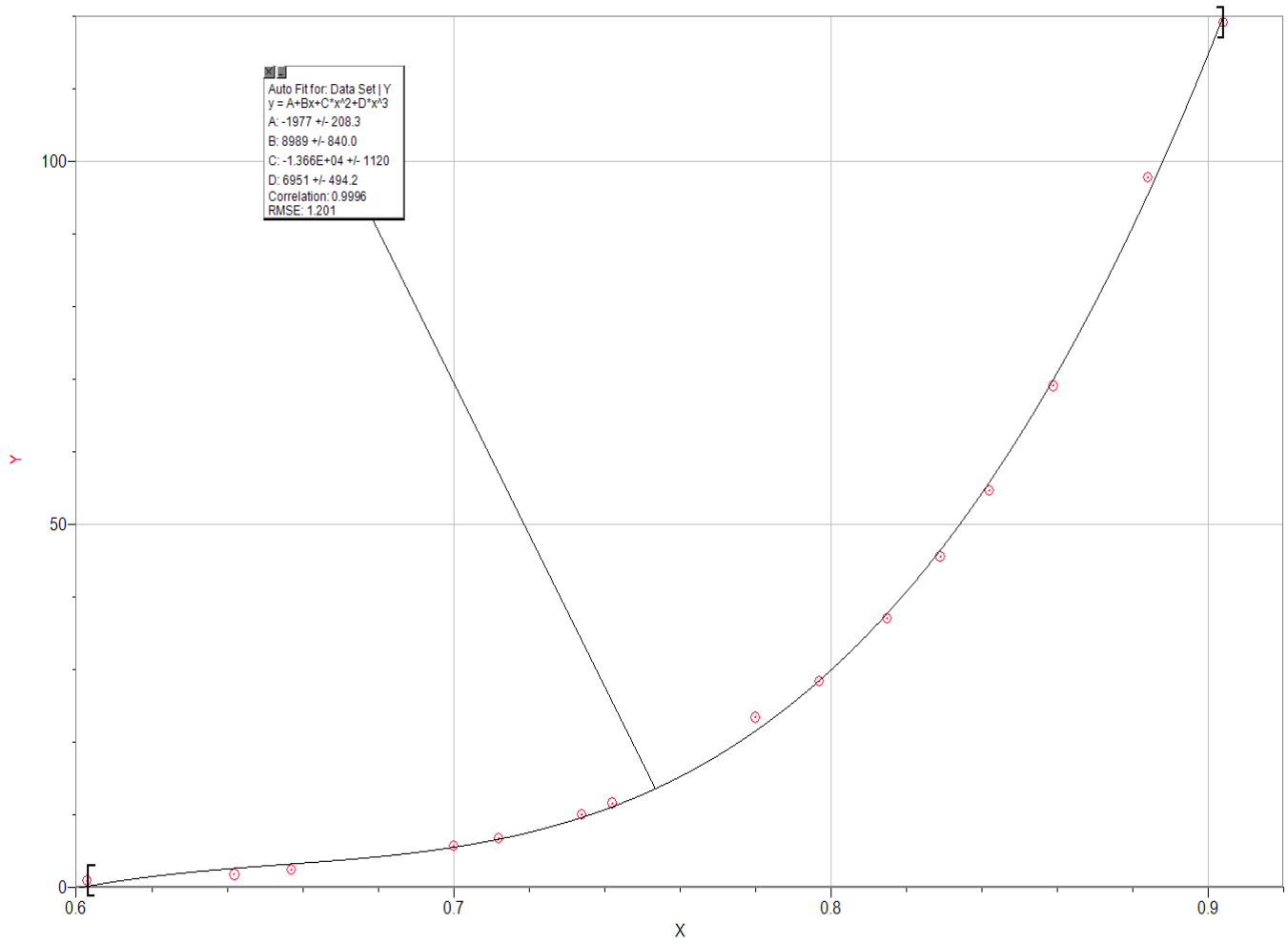


| | Data Set | |
|----|----------|--------|
| | X | Y |
| 1 | 0.7 | 5.64 |
| 2 | 0.712 | 6.66 |
| 3 | 0.734 | 9.995 |
| 4 | 0.742 | 11.55 |
| 5 | 0.78 | 23.38 |
| 6 | 0.797 | 28.33 |
| 7 | 0.815 | 37.06 |
| 8 | 0.829 | 45.5 |
| 9 | 0.842 | 54.7 |
| 10 | 0.859 | 69.07 |
| 11 | 0.884 | 97.82 |
| 12 | 0.904 | 119.19 |
| 13 | 0.603 | 0.91 |
| 14 | 0.642 | 1.72 |
| 15 | 0.657 | 2.36 |

FIG. 2. Diode Forward

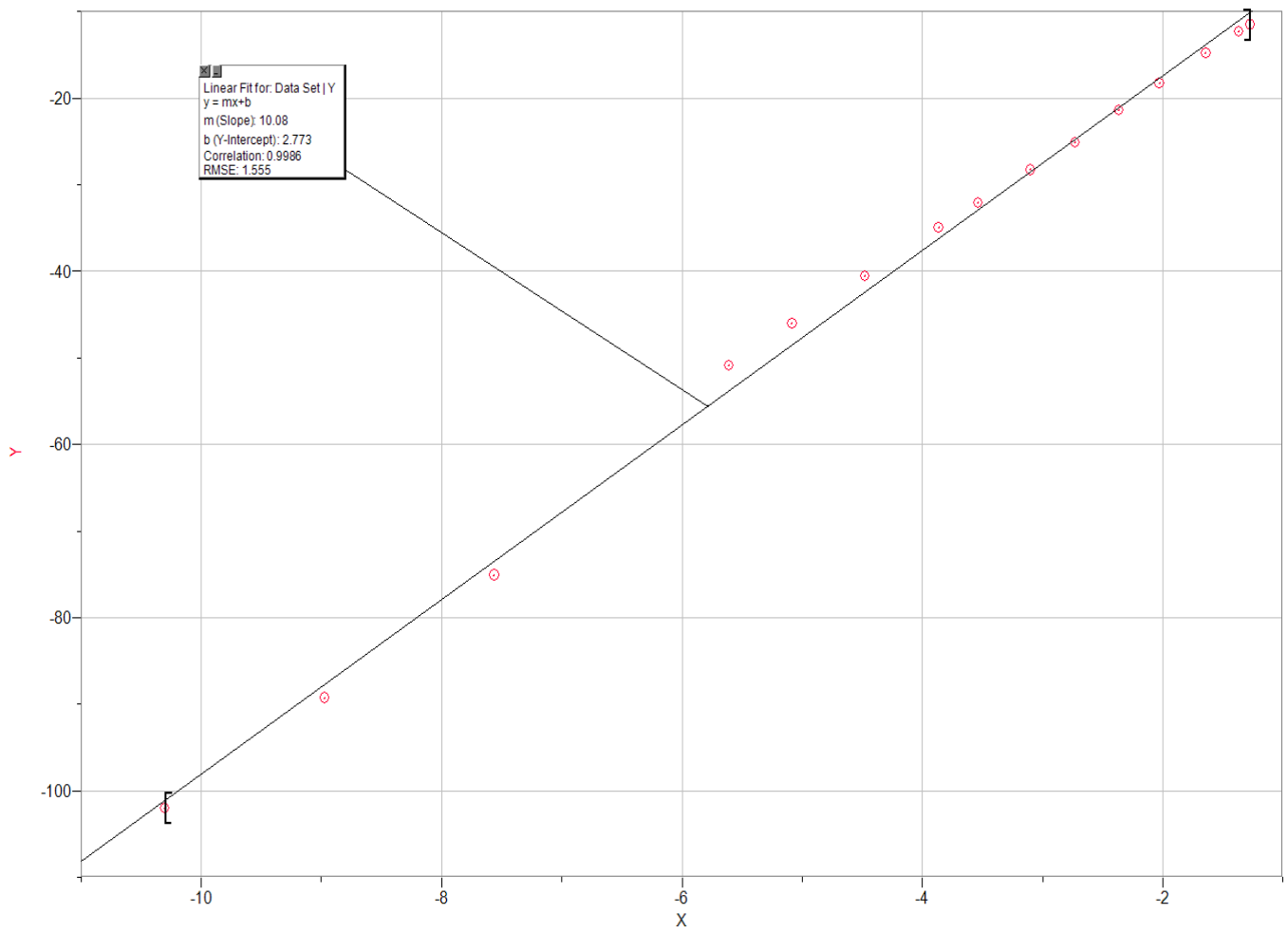


| | Data Set | |
|----|----------|-------|
| | X | Y |
| 1 | -1.27 | -11.5 |
| 2 | -1.365 | -12.3 |
| 3 | -1.64 | -14.8 |
| 4 | -2.027 | -18.3 |
| 5 | -2.365 | -21.4 |
| 6 | -2.73 | -25.1 |
| 7 | -3.101 | -28.3 |
| 8 | -3.532 | -32.1 |
| 9 | -3.863 | -35 |
| 10 | -4.478 | -40.6 |
| 11 | -5.083 | -46 |
| 12 | -5.61 | -50.9 |
| 13 | -7.56 | -75.1 |
| 14 | -8.97 | -89.3 |
| 15 | -10.3 | -102 |

FIG. 3. Diode Backward

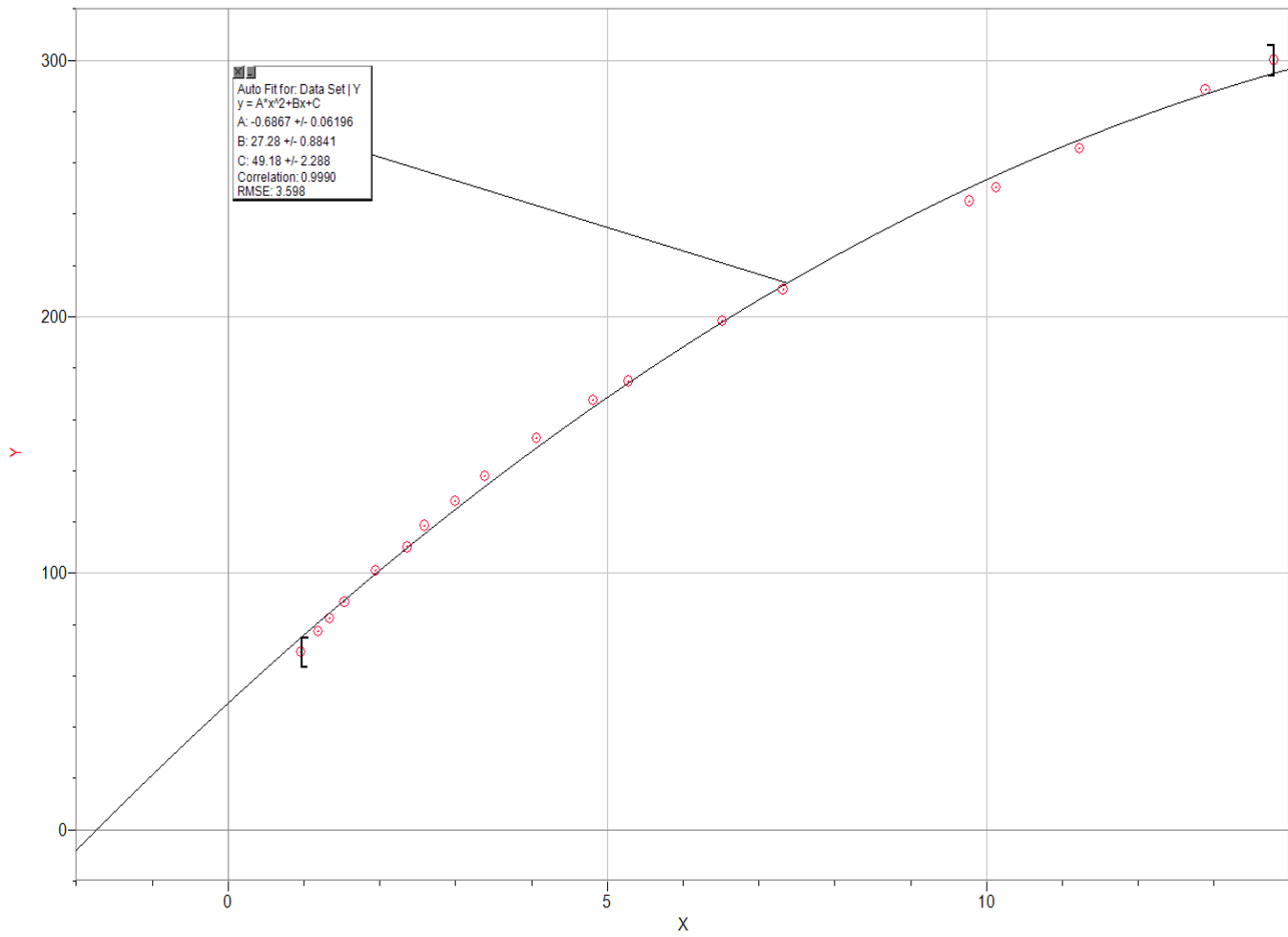


| | Data Set | |
|----|----------|---------|
| | X | Y |
| 1 | 0.963 | 69.225 |
| 2 | 1.185 | 77.147 |
| 3 | 1.341 | 82.451 |
| 4 | 1.536 | 88.678 |
| 5 | 1.945 | 101.1 |
| 6 | 2.367 | 110.1 |
| 7 | 2.588 | 118.52 |
| 8 | 2.992 | 128.159 |
| 9 | 3.39 | 137.7 |
| 10 | 4.065 | 152.478 |
| 11 | 4.815 | 167.567 |
| 12 | 5.285 | 174.772 |
| 13 | 6.515 | 198.181 |
| 14 | 7.32 | 210.625 |
| 15 | 9.78 | 245.03 |
| 16 | 10.13 | 250.3 |
| 17 | 11.23 | 265.45 |
| 18 | 12.89 | 288.5 |
| 19 | 13.79 | 300.01 |

FIG. 4. Lamp Forward

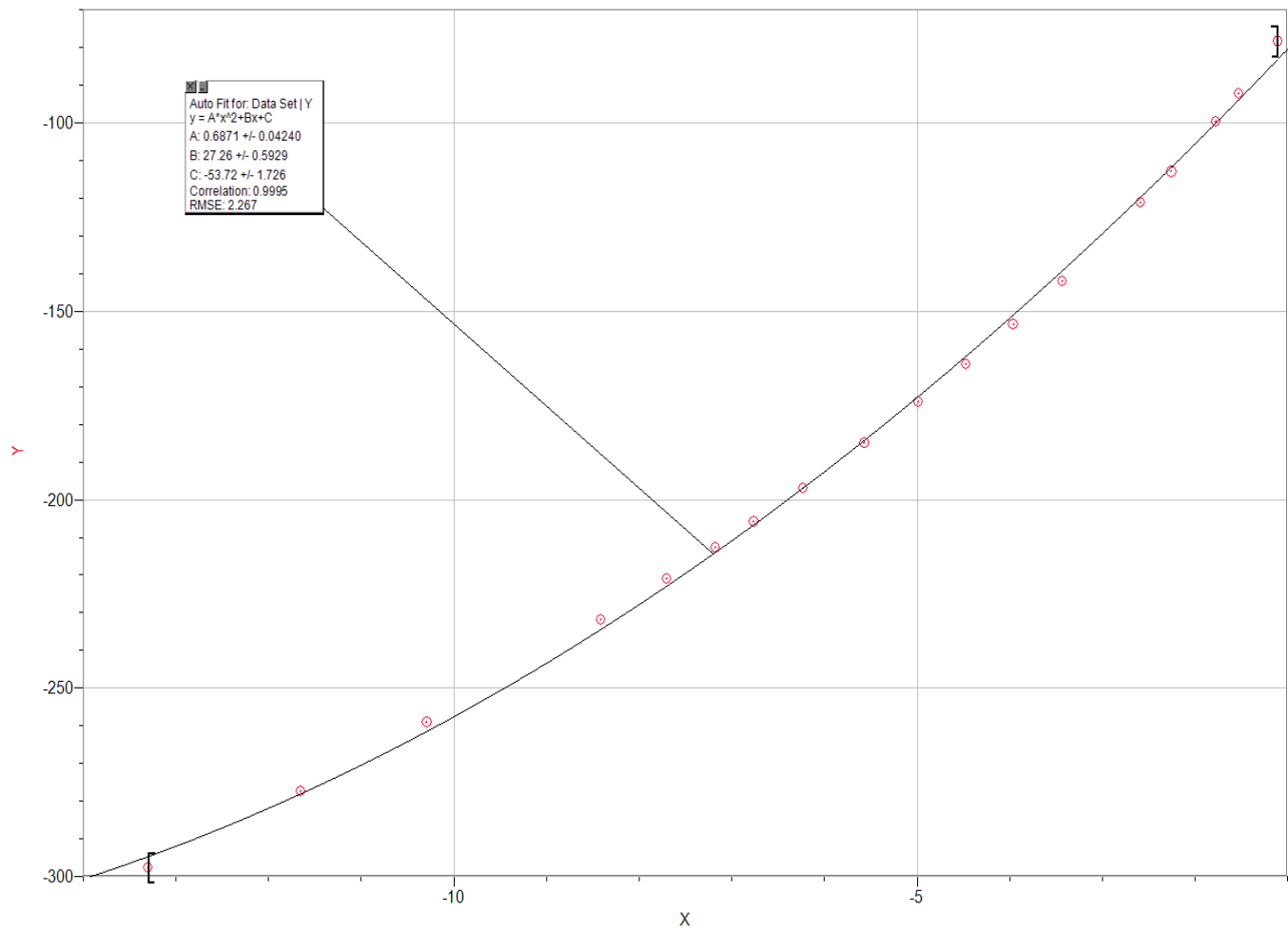


| | Data Set | |
|----|----------|---------|
| | X | Y |
| 1 | -1.103 | -78.32 |
| 2 | -1.524 | -92.13 |
| 3 | -1.772 | -99.57 |
| 4 | -2.253 | -112.94 |
| 5 | -2.588 | -121.21 |
| 6 | -3.429 | -141.96 |
| 7 | -3.96 | -153.4 |
| 8 | -4.47 | -163.96 |
| 9 | -4.985 | -174.16 |
| 10 | -5.567 | -185.03 |
| 11 | -6.23 | -196.87 |
| 12 | -6.76 | -205.93 |
| 13 | -7.18 | -212.74 |
| 14 | -7.7 | -221.03 |
| 15 | -8.41 | -231.83 |
| 16 | -10.29 | -259.09 |
| 17 | -11.65 | -277.5 |
| 18 | -13.3 | -297.72 |

FIG. 5. Lamp Backward

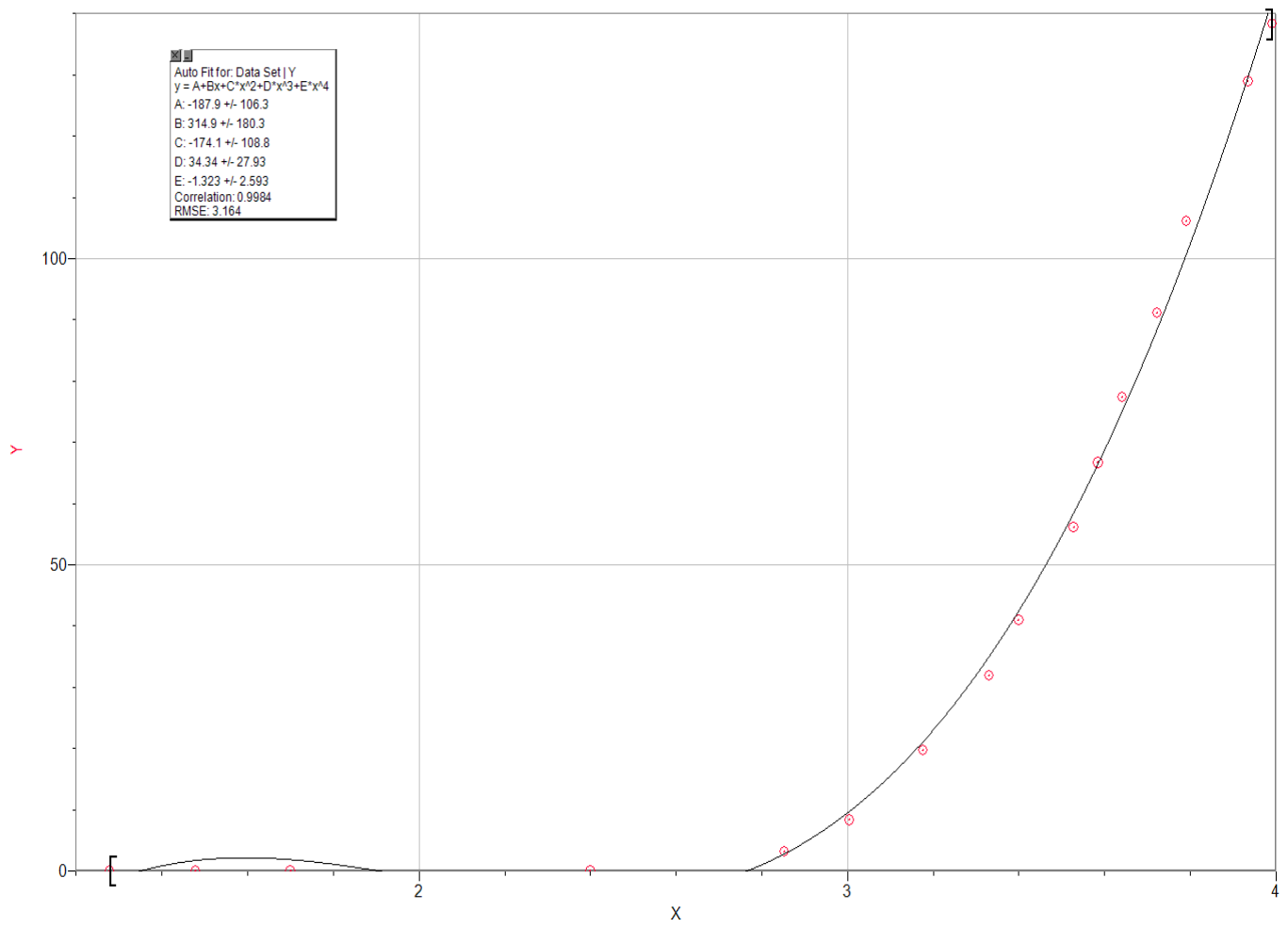


| | Data Set | |
|----|----------|--------|
| | X | Y |
| 1 | 1.278 | 0 |
| 2 | 1.478 | 0 |
| 3 | 1.7 | 0 |
| 4 | 2.4 | 0.02 |
| 5 | 2.853 | 3.148 |
| 6 | 3.004 | 8.276 |
| 7 | 3.177 | 19.63 |
| 8 | 3.33 | 31.832 |
| 9 | 3.4 | 40.937 |
| 10 | 3.528 | 56.115 |
| 11 | 3.585 | 66.652 |
| 12 | 3.642 | 77.286 |
| 13 | 3.722 | 91.1 |
| 14 | 3.791 | 106.12 |
| 15 | 3.935 | 128.95 |
| 16 | 3.992 | 138.3 |

FIG. 6. LED Forward

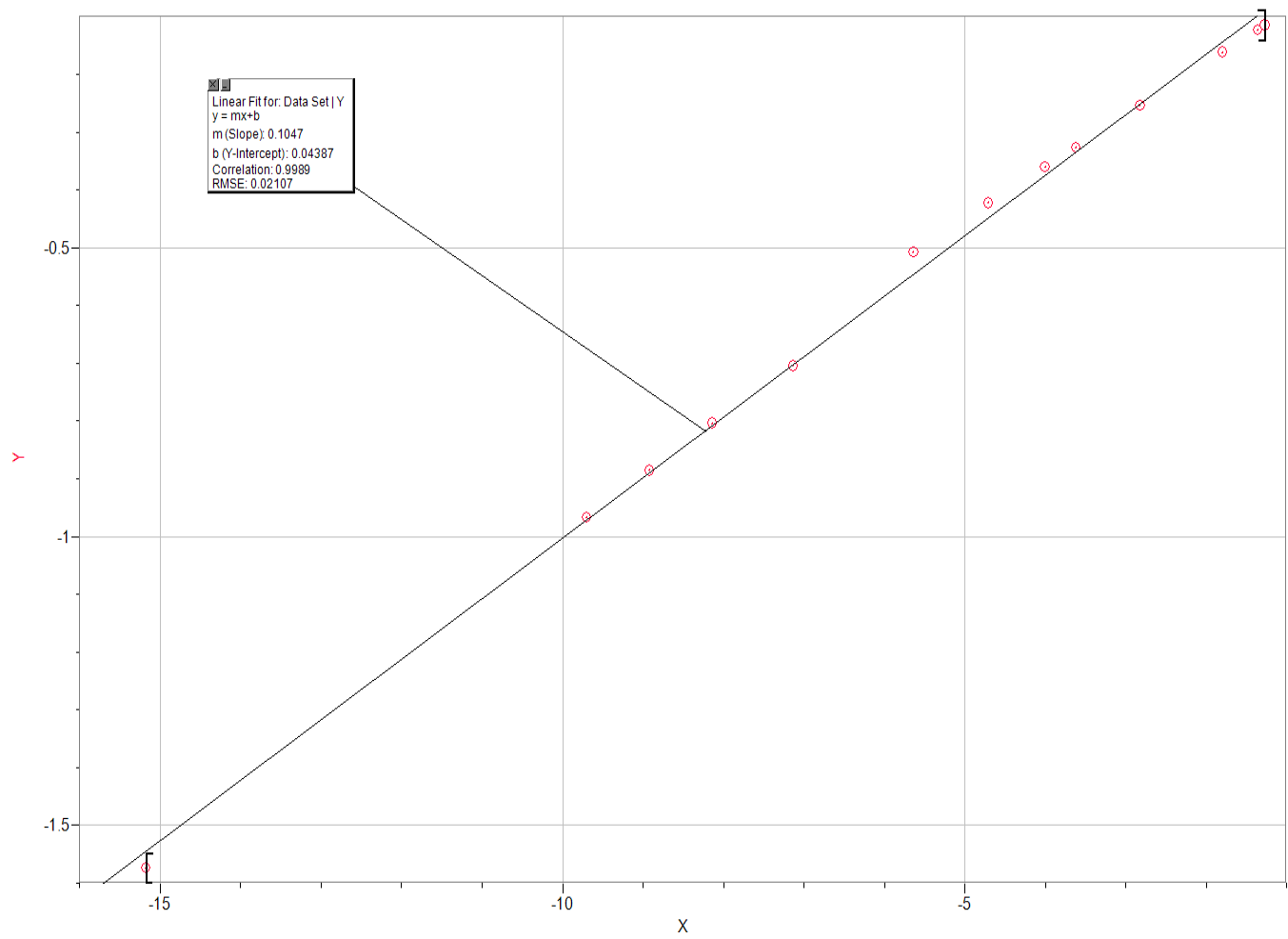


| | Data Set | |
|----|----------|--------|
| | X | Y |
| 1 | -1.269 | -0.115 |
| 2 | -1.362 | -0.123 |
| 3 | -1.795 | -0.162 |
| 4 | -2.82 | -0.254 |
| 5 | -3.62 | -0.327 |
| 6 | -4.002 | -0.36 |
| 7 | -4.704 | -0.423 |
| 8 | -5.636 | -0.508 |
| 9 | -7.13 | -0.705 |
| 10 | -8.14 | -0.804 |
| 11 | -8.92 | -0.886 |
| 12 | -9.7 | -0.967 |
| 13 | -15.18 | -1.574 |

FIG. 7. LED Backward (micro amps)

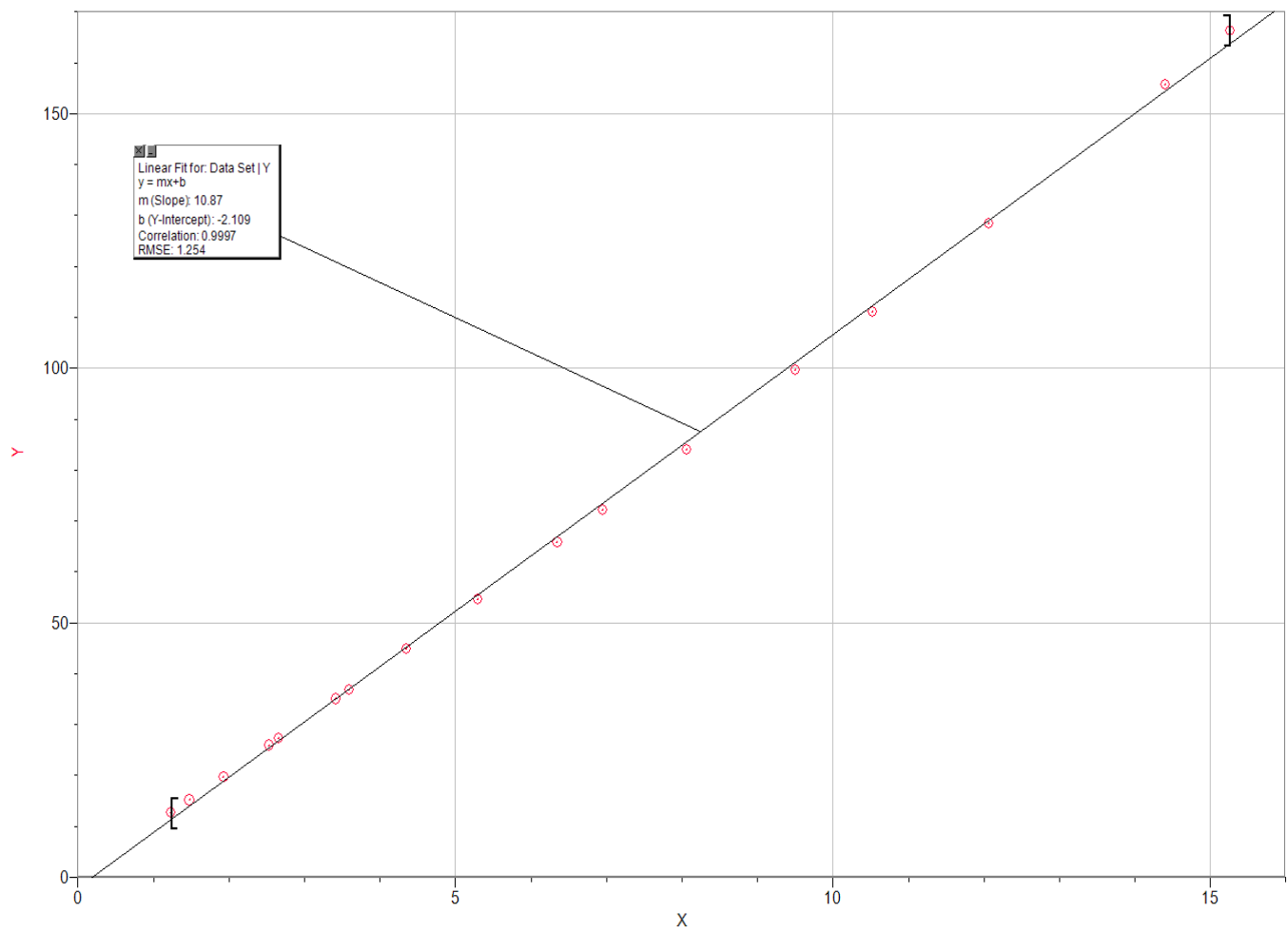

| | Data Set | |
|----|----------|---------|
| | X | Y |
| 1 | -1.245 | -12.71 |
| 2 | -1.33 | -13.6 |
| 3 | -1.75 | -17.97 |
| 4 | -2.368 | -24.27 |
| 5 | -3.004 | -30.78 |
| 6 | -3.755 | -38.47 |
| 7 | -4.133 | -42.48 |
| 8 | -4.569 | -47.1 |
| 9 | -5.14 | -52.9 |
| 10 | -5.59 | -57.75 |
| 11 | -6.177 | -63.62 |
| 12 | -6.82 | -70.66 |
| 13 | -7.89 | -82.32 |
| 14 | -8.75 | -91.44 |
| 15 | -9.59 | -100.7 |
| 16 | -10.26 | -108.37 |

FIG. 8. Resistor Forward

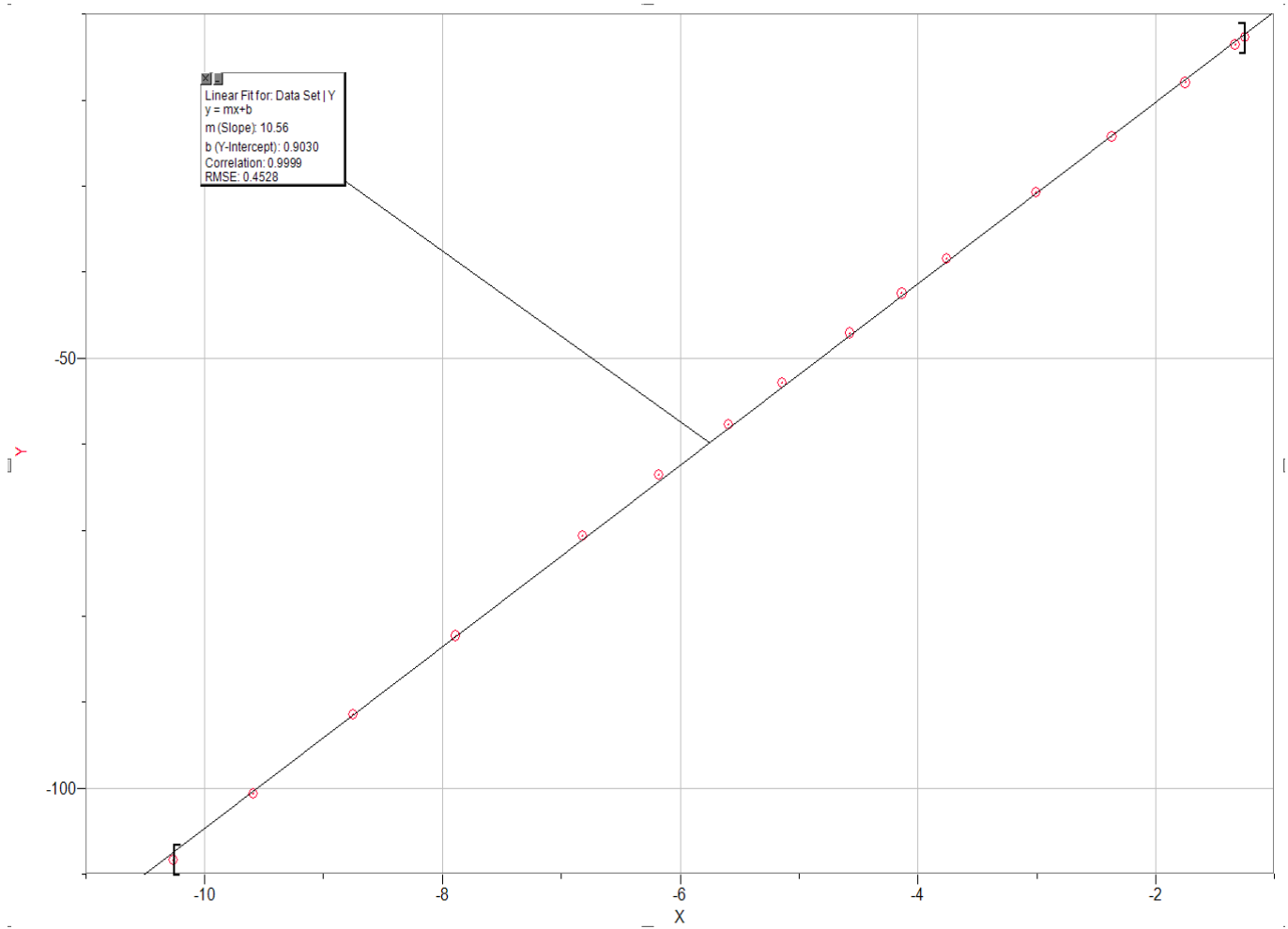

| | Data Set | |
|----|----------|--------|
| | X | Y |
| 1 | 1.23 | 12.62 |
| 2 | 1.478 | 15.13 |
| 3 | 1.931 | 19.72 |
| 4 | 2.536 | 25.9 |
| 5 | 2.655 | 27.25 |
| 6 | 3.413 | 35.02 |
| 7 | 3.59 | 36.86 |
| 8 | 4.351 | 44.79 |
| 9 | 5.294 | 54.63 |
| 10 | 6.352 | 65.72 |
| 11 | 6.95 | 72.07 |
| 12 | 8.06 | 84.01 |
| 13 | 9.5 | 99.65 |
| 14 | 10.53 | 111.07 |
| 15 | 12.07 | 128.44 |
| 16 | 14.4 | 155.77 |
| 17 | 15.26 | 166.35 |

FIG. 9. Resistor Backward